

# Random Number Geneeration Using Shift Registers

Ladva Umanshiva  
AI22BTECH11016

## Aim

To design and create a circuit, which dispalys a series of random numbers, on a seven segment diplay. (Frequency of display depends upon the components used.

## COMPONENTS USED

Component	Value	Quantity
Breadboard		1
Seven Segment Diplay	Common Anode	1
Decoder	7447	1
Flip Flop	7474	2
X-OR Gate	7486	1
555 IC		1
Resistor	1 K $\Omega$	1
Capacitor	100 nF	1
Capacitor	10 nF	1
Jumper Wires		

TABLE 0  
COMPONENTS USED

## DESCRIPTION

1) Build the CLOCK circuit as shown below.

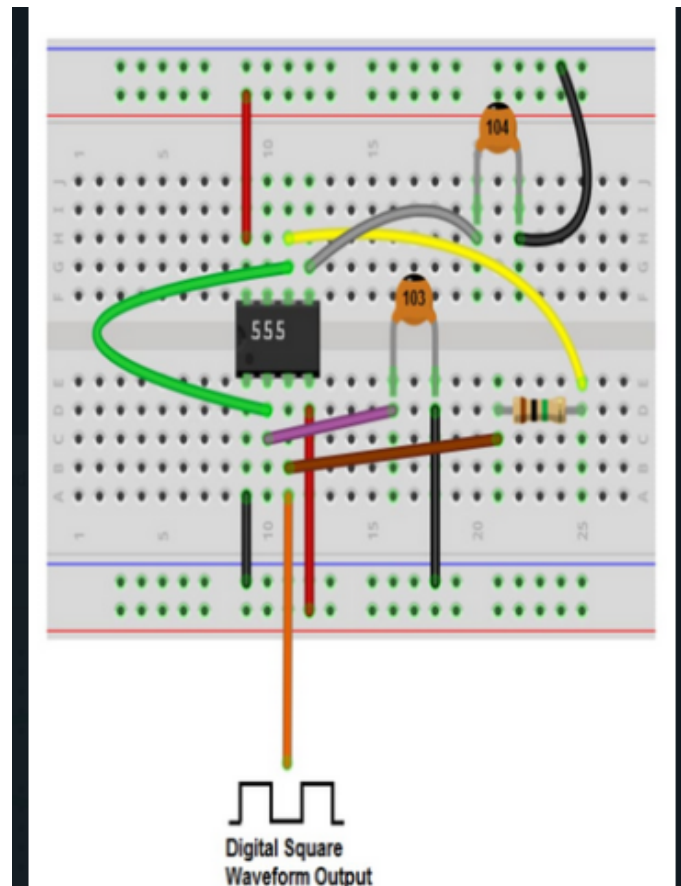


Fig. 1. CLOCK circuit diagram of breadboard

- The wave form output of clock circuit is used as input in the flip-flop circuit containing two 7474 IC's, one XOR gate and one decoder.
- Both the circuits are then connected with a seven segment display in which output is shown. Random numbers will appear on the display.

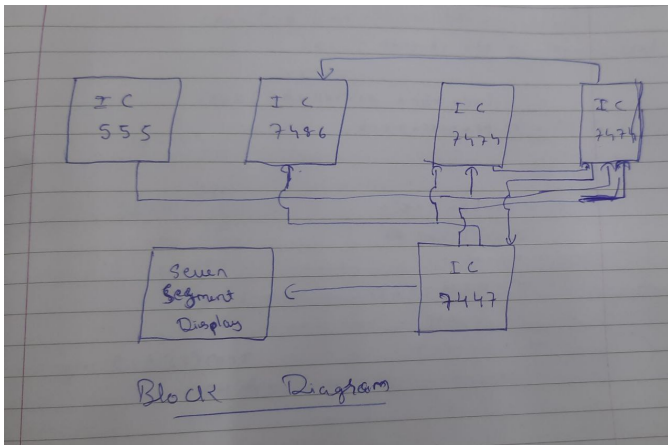


Fig. 3. Block Diagram

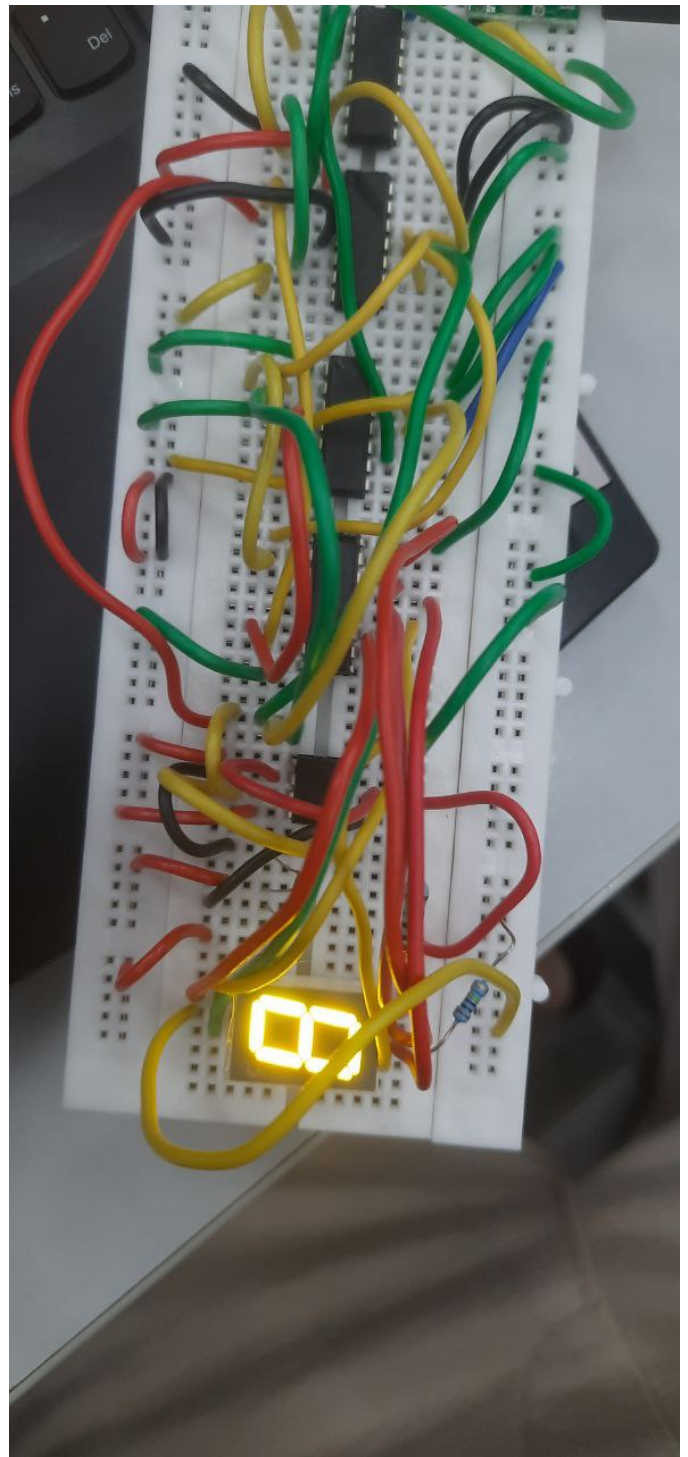


Fig. 3. Output 1

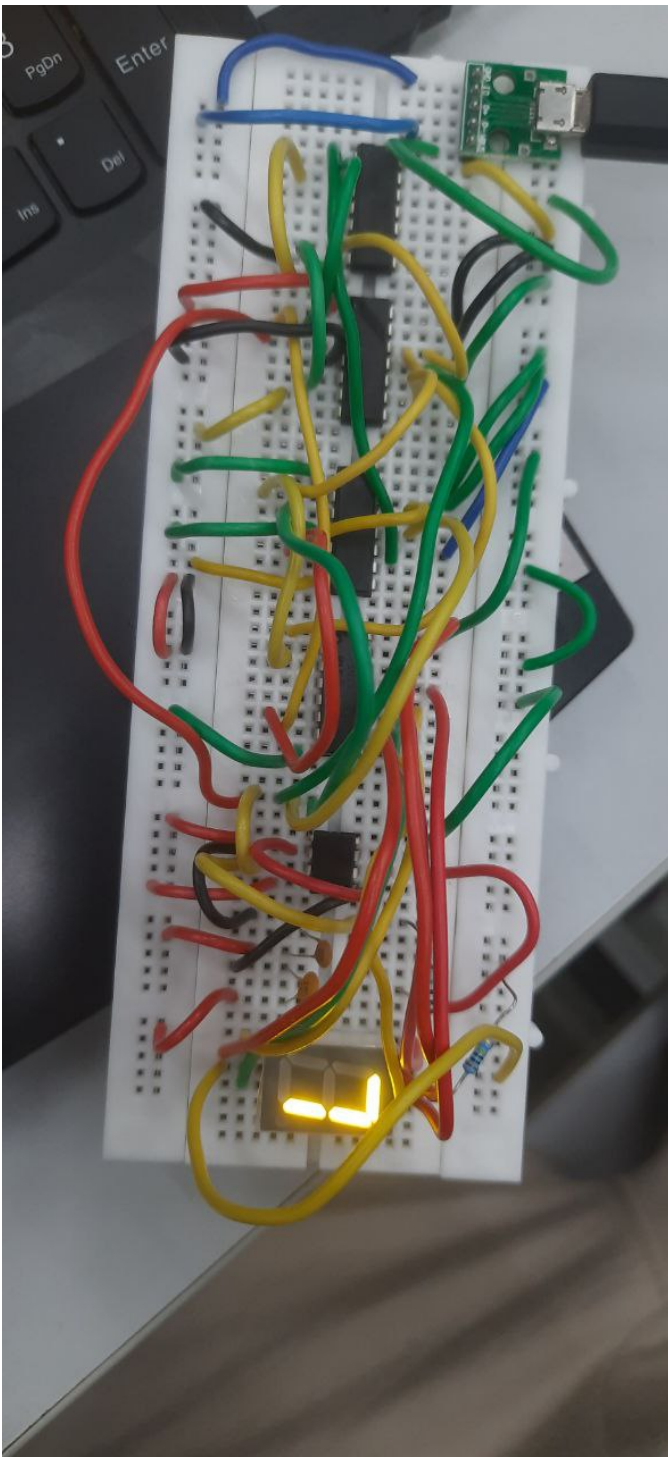


Fig. 3. Output 2